

# Projet LG-3 Lefranc Joaquim, Skoda Jérôme



#### **Tableaux de Karnaugh**

## Table AddUnit Table DOUBLE INTERUPT

	00	01	11	10
00	No	No	No	No
01	No	No	No	No
11	Yes	No	No	Yes
10	No	No	No	No

	00	01	11	10
00	No	No	No	No
01	No	No	No	No
11	No	No	No	No
10	No	No	Yes	Yes

### Table JUMP

#### Table LOAD

	00	01	11	10
00	Yes	No	No	No
01	Yes	No	No	No
11	Yes	No	Yes	No
10	Yes	No	No	No

	00	01	11	10
00	No	No	No	Yes
01	No	No	No	Yes
11	No	No	Yes	No
10	No	No	Yes	Yes

## Table LoadMem

<del>_</del> ,		<b>C</b> -		
lab	10	5	I ( )	RF
IGO				

	00	01	11	10
00	No	No	Yes	Yes
01	No	No	Yes	Yes
11	No	No	Yes	No
10	No	No	Yes	Yes

	00	01	11	10
00	No	No	Yes	No
01	No	No	Yes	No
11	No	No	No	No
10	No	No	Yes	No

## Table WriteR7

## Table WriteReg

	00	01	11	10
00	No	No	No	No
01	Yes	No	No	No
11	No	No	Yes	No
10	No	No	No	No

	00	01	11	10
00	No	Yes	No	Yes
01	Yes	Yes	No	Yes
11	No	Yes	Yes	Yes
10	-	Yes	No	Yes